

ELECTRONICS

2006

FIRST PAPER

Full Marks : 200

Time : 3 hours

The figures in the margin indicate full marks
for the questions

1. (a) Consider a piece of uniformly doped germanium with 10^{15} cm^{-3} shallow acceptors. Calculate the temperature for which the electron density equals the ionized acceptor density. Ignore the temperature dependence of the energy bandgap and use $E_g = 0.67 \text{ eV}$. 10
- (b) Consider a silicon metal-semiconductor junction with an n -type doping given by


$$N_d = N_o \frac{x}{d} \quad \text{for } x < d$$

$$N_d = N_o \quad \text{for } x > d$$

Calculate the voltage and the capacitance corresponding to a depletion layer width of $2d$. Use $N_o = 4 \times 10^{16} \text{ cm}^{-3}$, $d = 400 \text{ nm}$, the area = 10^{-4} cm^{-2} and $\phi_i = 0.8 \text{ V}$. 10

(2)

 
2. A MOS capacitor is made from Si. When V_G is applied to the gate of the capacitor, the band diagram looks as shown below. Oxide and metal parts are not shown. Answer the questions :



- (a) Is the applied voltage V_G positive or negative? Explain.
- (b) Is the semiconductor *p*-type or *n*-type? What is the doping concentration?
- (c) Calculate the number of electrons and holes in the bulk of the semiconductor.
- (d) Calculate the number of electrons and holes near the surface of the semiconductor.
- (e) Is the semiconductor under depletion, inversion or in flat-band condition? 25

(3)

 3. The mask set for a simple rectangular p - n junction diode is shown below. The diode is formed in a p -type substrate :




- (a) How many masks are required to fabricate the structure as shown?
- (b) Draw a picture of the layout for the diode, which results when a worst-case misalignment of $3\ \mu\text{m}$ occurs in x -direction on each mask level. Assume that the contact level is aligned to the diffusion level and the metal level is aligned to the contact level.
- (c) What will happen, if the contact hole is $6\ \mu\text{m} \times 6\ \mu\text{m}$ square? Will the device work?

15

4. Use the small-signal model and nodal analysis to show that the output impedance for the MOS Wilson current mirror shown at right is given by $R_{out} \approx r_{ds2}(1 + g_{m2} r_{ds3})$, neglecting body effect :

30

 


5. (a) For the circuit shown below, find the minimum DC open-loop op-amp gain required in order for the closed-loop gain to be accurate within 0.5%. Use $R_1 = 1 \text{ k}\Omega$, $R_2 = 19 \text{ k}\Omega$.

10


- (b) If the op-amp has a unity gain bandwidth of $f_T = 1 \text{ GHz}$, find the % settling error if the op-amp is allowed to settle for 10 nsec.

10

 

(Continued)

 6. (a) On the layout diagram below, indicate the metal connections required to implement the function $F = A \oplus B$. Assume that both inverted and non-inverted inputs are available and label each polygate with the input used: 15



- (b) Draw the schematic diagram for the logic gate above. 15

7. (a) All microprocessors have something that is called a program counter. What is this?

- (b) Give the machine code as a 4-digit hex value for the instruction :

bsf 0x14F,4

- (c) Whether the machine code 0x31F2 represents instruction? (Use w or f for the destination, and ACCESS or BANKED to represent the value of a bit.)

(d) For a 20 MHz clock, how long does it take to execute the following instructions? (Give the answer in microseconds.)


```
movff 0x230, 0x110  
clrf 0x002, f
```

(e) What location in program memory is the first instruction fetched from after a reset?

20


8. Consider the amplifier circuit in the figure. When the source voltage V_s has zero d.c. component, the output d.c. voltage V_o is 5 V. Let both BJTs have $\beta = 50$. Determine the d.c. voltages at all the nodes and the d.c. emitter currents of Q_1 and Q_2 :

20

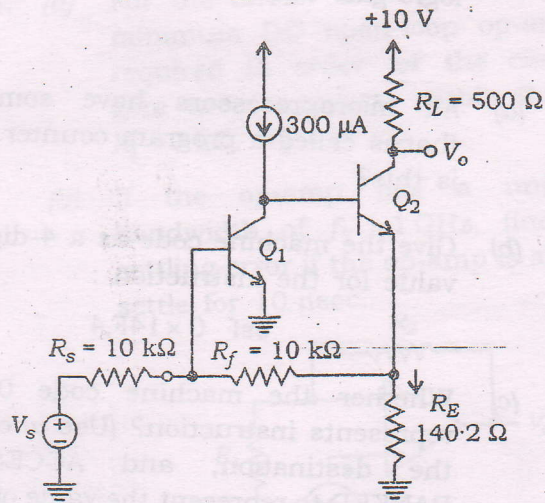

 9. In the saturation region, the MOSFET shown in the circuit below has an i_D - v_{DS} relation given by $i_D = \frac{K}{2}(v_{GS} - V_T)^3$, where

$$K = \frac{1}{2} \text{ mA/V}^3 \text{ and } V_T = 2 \text{ V.}$$



Find the relation between R_1 and R_2 that will fix the output bias voltage at 6 V.

10

10. A small source is added to the circuit above as shown in the figure. Draw a small-signal model for the circuit that can be used to analyze the gain $G = V_{out}/V_{in}$ and calculate the small signal gain :

10

