

2014

ELECTRONICS

FIRST PAPER

Full Marks : 200

Time : 3 hours

The figures in the margin indicate full marks  
for the questions

1. (a) Draw the  $I$ - $V$  characteristics of a  $p$ - $n$  junction diode—
  - (i) under dark condition;
  - (ii) when exposed to solar light. 3+3=6
- (b) Explain in detail both the characteristics physically. 10
- (c) What is Fermi level? Derive the expressions for Fermi level in intrinsic,  $P$ -type and  $N$ -type semiconductors. 9
2. (a) Explain the following :
  - (i) Mobility
  - (ii) Conductivity
  - (iii) Energy gap
  - (iv) Intrinsic concentrationAlso give the reason about the variation of these parameters with temperature.

4+4=8

( 2 )

(b) When a diode is reverse biased with 6 V, it has a junction capacitance of 10 pF. When the reverse bias increases to 10 V, the capacitance drops to 8.43 pF. Find whether the junction is abrupt or graded. 7

(c) Explain the  $I$ - $V$  characteristics of tunnel diode with the help of energy band diagram. 10

3. (a) Design a voltage divider circuit in Fig. 1 given below to operate from 12 V supply. The bias conditions are to be  $V_{CE} = 3V$ ,  $V_E = 5V$  and  $I_C = 1\text{ mA}$ . 10

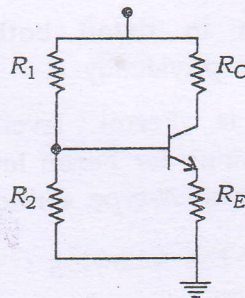


Fig. 1

(b) Draw the circuit diagram for a BJT differential amplifier using a single polarity supply. Explain the d.c. and a.c. operations of each circuit. Write equations for voltage gain and input, output impedance for a differential amplifier. 10



- (c) A Zener diode shunt regulator has to supply a load current which varies from 0 to 200 mA at 10 V. The input to the regulator varies from 15 V to 20 V. Assume that Zener diode voltage stabilizes at a minimum current of 10 mA. Calculate the value of the series resistor and power rating of the Zener diode.

5

4. (a) Write in short on the following observed in BJT :

5×3=15

- (i) Base width modulation
- (ii) Emitter band gap narrowing
- (iii) Current crowding

- (b) For the transistor amplifier shown in Fig. 2 below, find  $A_I$ ,  $A_V$ ,  $A_{VS}$ ,  $R_o$  and  $R_i$ , if  $h$  parameters are as

$$h_{ie} = 1.1 \text{ k}\Omega, h_{re} = 2.5 \times 10^{-4}$$

$$h_{fe} = 50, h_{oe} = 25 \times 10^{-6} \text{ S}$$

10

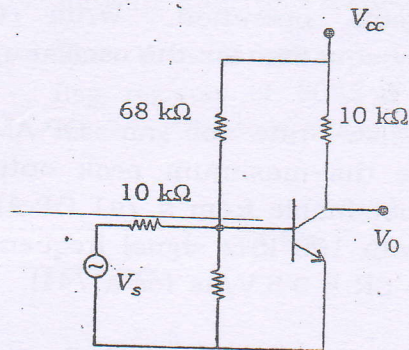


Fig. 2

5. (a) Discuss briefly about multi-emitter transistor (MET) and its method of fabrication. Also mention the application of MET. 6+3=9
- (b) Explain MOS capacitor and its fabrication method. Compare MOS capacitor with reverse biased P-N junction used as capacitor. 5+3=8
- (c) Why stick diagrams are important in integrating devices in microelectronics? Discuss about various color coding schemes in stick diagram. 5+3=8
6. (a) Draw the circuit diagram of an OP-AMP Wien bridge oscillator. Sketch the oscillator output waveforms and explain the circuit operation. Write the frequency equation for the oscillator. 12
- (b) Define slew rate of an OP-AMP. Calculate the maximum peak output voltage obtainable from a 741 OP-AMP circuit with 100 kHz signal frequency. [Assume  $SR = 0.5 \text{ V}/\mu\text{s}$  for a 741]. 5
- (c) What are different layout design and analysis tools? Discuss CAD tools scheme in detail. 8



7. (a) List in detail the steps involved in fabricating a monolithic IC. Illustrate the steps with suitable diagrams wherever necessary. 15
- (b) Define sheet resistance  $R_s$ . What is the total length required to fabricate a 20-k $\Omega$  resistor whose width is 20 $\mu\text{m}$ , if  $R_s = 200 \Omega/\text{square}$ ? What is the width required to fabricate a 5-k $\Omega$  resistor whose length is 25  $\mu\text{m}$ ? 10
8. (a) What do you understand by addressing mode of a computer or processor? Write about various addressing modes of 8085  $\mu\text{P}$  with two examples for each one of them. 10
- (b) Discuss in detail about hardware and software interrupts available in 8085  $\mu\text{P}$ . 8
- (c) Show the arrangement of flag bits in the flag register of 8085  $\mu\text{P}$ . Explain the meaning of each one of them. 7

---

\*\*\*